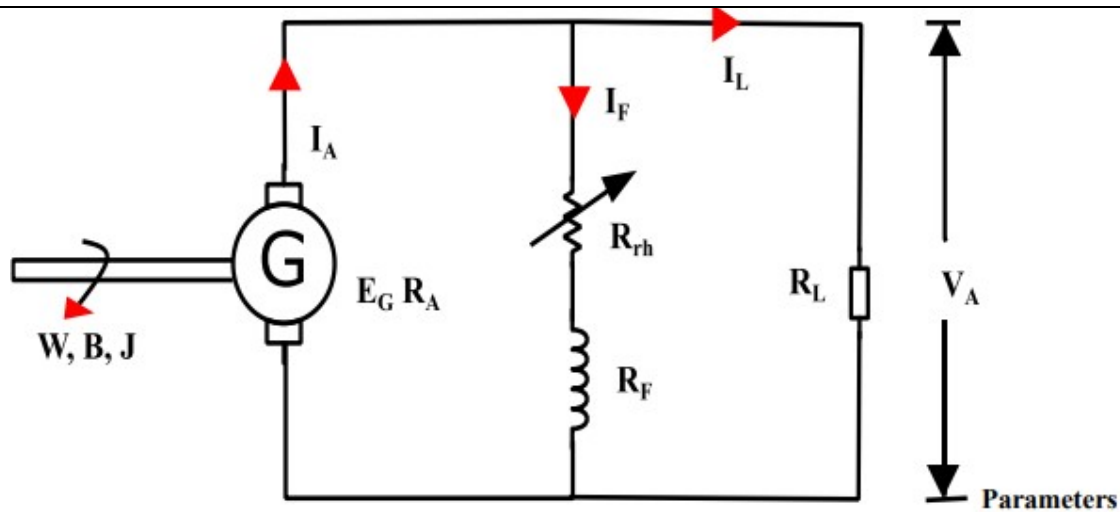


TITLE OF THE EXERCISE: DC shunt generator

DATE:06/10/20

AIM: To develop and Simulate mathematical dynamic modal of DC shunt generator under magnetic saturation and also analyze with theoretical results.

TOOL USED: MATLAB and SIMULINK



ELECTRICAL CIRCUIT: PARAMETERS

USED FOR THE STUDY:

Armature resistance $R_A = 0.24$ ohms

Armature winding inductance $L_A = 0.018$ H

Shunt field winding resistance $R_F = 111$ ohms

Shunt field winding inductance $L_F = 10$ H

Shunt field Rheostat Resistance $R_{rh} = 25$ ohms

Load resistance $R_L = 100000$ ohms

Rated Voltage $V_A = 125$ volts

Rated Current $I_A = 16$ amps

Rated power $P = 2$ KW

Rated Speed $\omega_m = 183$ rad/sec


Speed $\omega_{mo} = 209.5$ rad/sec (speed at Give field current and voltage Data)

Carbon brush Voltage Drop $V_{brush} = 2$ volt

Field Current	Generated Voltage Ego
0	7.5
0.05	12
0.1	20
0.13	24
0.18	32
0.22	40
0.26	48
0.32	59
0.36	66
0.4	74
0.47	86
0.54	97
0.575	102.5
0.61	107.5

0.64	112
0.68	117
0.71	121
0.74	125
0.78	130
0.82	135
0.86	140
0.9	143
0.93	146
1	152
1.1	158
1.2	164
1.3	168
1.4	172
1.5	175

Theoretical Analysis: The open circuit characteristics of the dc shunt motor is observed under two different speeds And the corresponding effect of varying If,Iar,wm,RL are noted.	
Calculations (Predetermination): $I_f = 1 \text{ A};$ $V_f = (R_f + R_{rh}) * I_f = (111 + 25) * 1 = 136 \text{ V};$ $I_L = 136 / (1E6) \text{ A} = 0.136 \text{ mA}$ $I_a = I_L + I_f = 1 + 0.000136 \text{ A} = 1.000136 \text{ A}$ Eg $= V_a + I_a R_a + V_b = 136 + 0.24 + 2 = 138.24 \text{ V}$ $\omega_m = (138.24 / 152) * 209.5 = 190.5 \text{ rad/sec};$ $K\phi = E_g / \omega_m = 0.7255 \text{ Vs}$ $T_e = K\phi * I_a = 0.7255 * 1.000136 = 0.7256 \text{ Nm}$	
Procedure for simulation study: - Step1-Write the coding for Initialize the input parameters and as per requirement of plots in m file and save it - Step 2-open new Simulink file and make mathematical modelling as per circuit diagram and save it - Step3-Run the m file first, after that run Simulink file - Step4-View the result in Scope - Step5- Again run m file and view the plots - Step6-Make various plots and write the Results	
Simulation Diagram and m.file coding : **Simulation rendered wave form:-**	

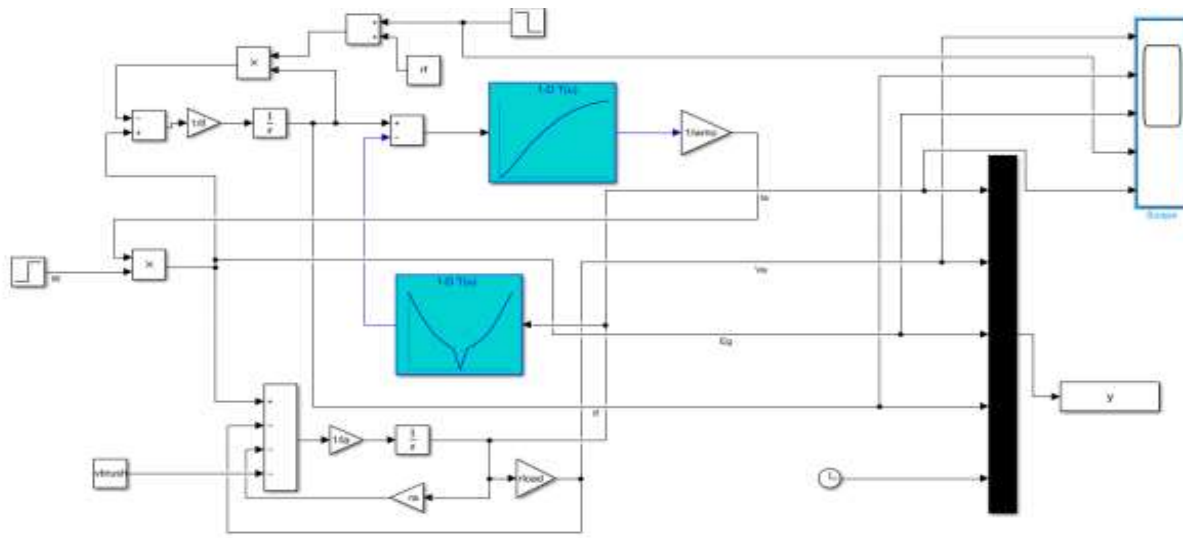

```

prated = 2000;
vrated = 125;
larated = 16;
wmrated = 1750*(2*pi)/60;
Trated = prated/wmrated;
ra = 0.24;
rf = 111;
rrh = 25;
la = 0.018;
lf = 10;
rload = 1e6;
j = 0.8;
vbrush = 2;
wmo = 2000*(2*pi)/60;

```

```

SHVP1 = [7.5 12 20 24 32 40 48 59 66 74 86 97 102.5 ...
107.5 112 117 121 125 130 135 140 143 146 152 158 164 168 172 175];

```

```

SHIP1 = [0 0.05 0.1 0.13 0.18 0.22 0.26 0.32 0.36 0.4 0.47 0.54 ...
0.575 0.61 0.64 0.68 0.71 0.74 0.78 0.82 0.86 0.9 0.93 1.0 1.1 ...
1.2 1.3 1.4 1.5];

```

```

plot(SHIP1,SHVP1);
la = [-40:5:40];
lar = 0.04*abs(atan(la)) + 0.0001*la.^2;

```

```


keyboard
subplot(4,1,1)
plot(y(:,5),y(:,4))
ylabel("If in A");
subplot(4,1,2)
plot(y(:,5),y(:,3))
ylabel("Eb in V");
subplot(4,1,3)
plot(y(:,5),y(:,1))
ylabel("Ia in A");


```

```
subplot(4,1,4)
plot(y(:,5),y(:,2))
ylabel("Va in V");
```

Results and Discussions:

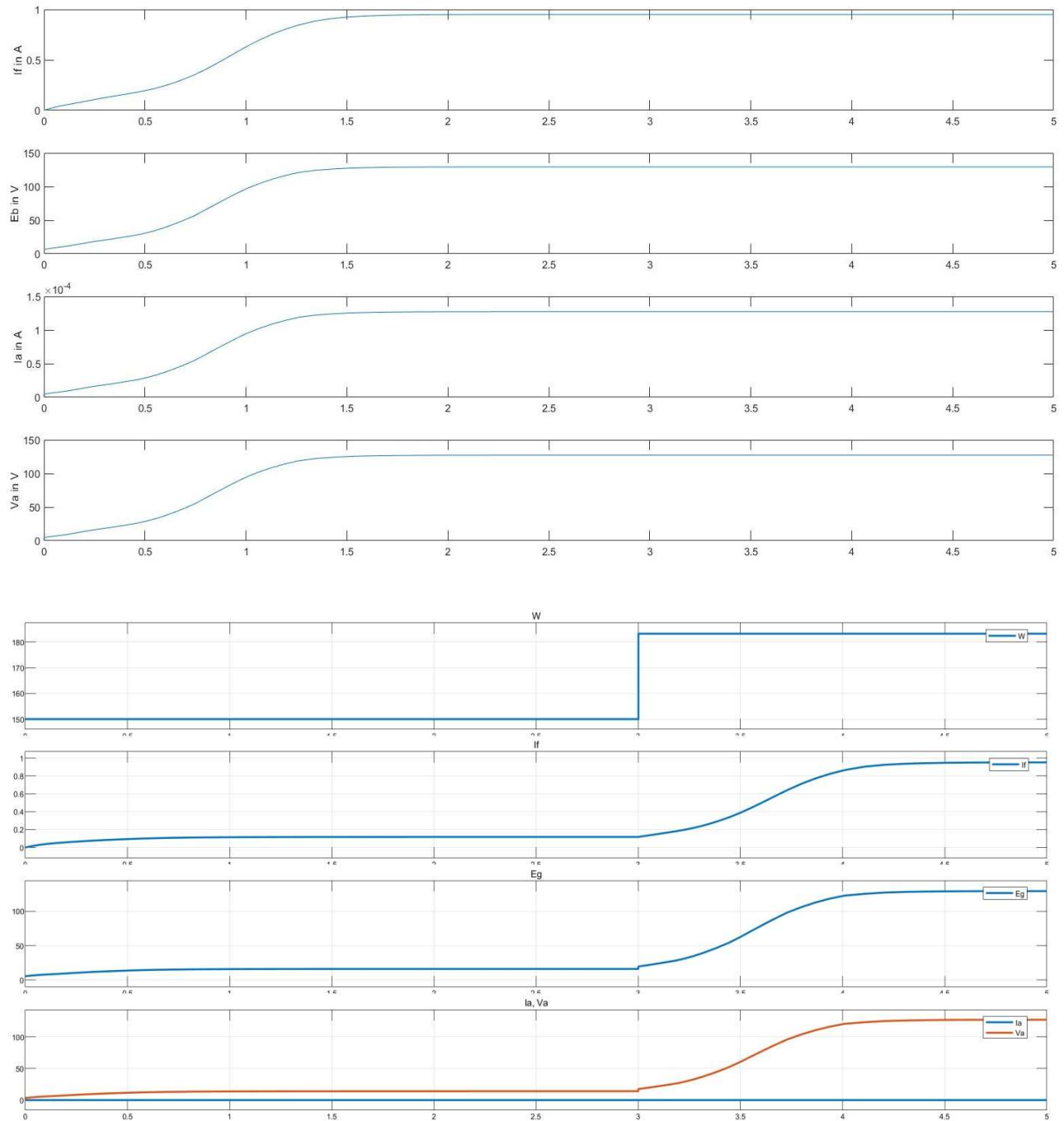This section contains both waveforms with respect to time along with the theoretical value.



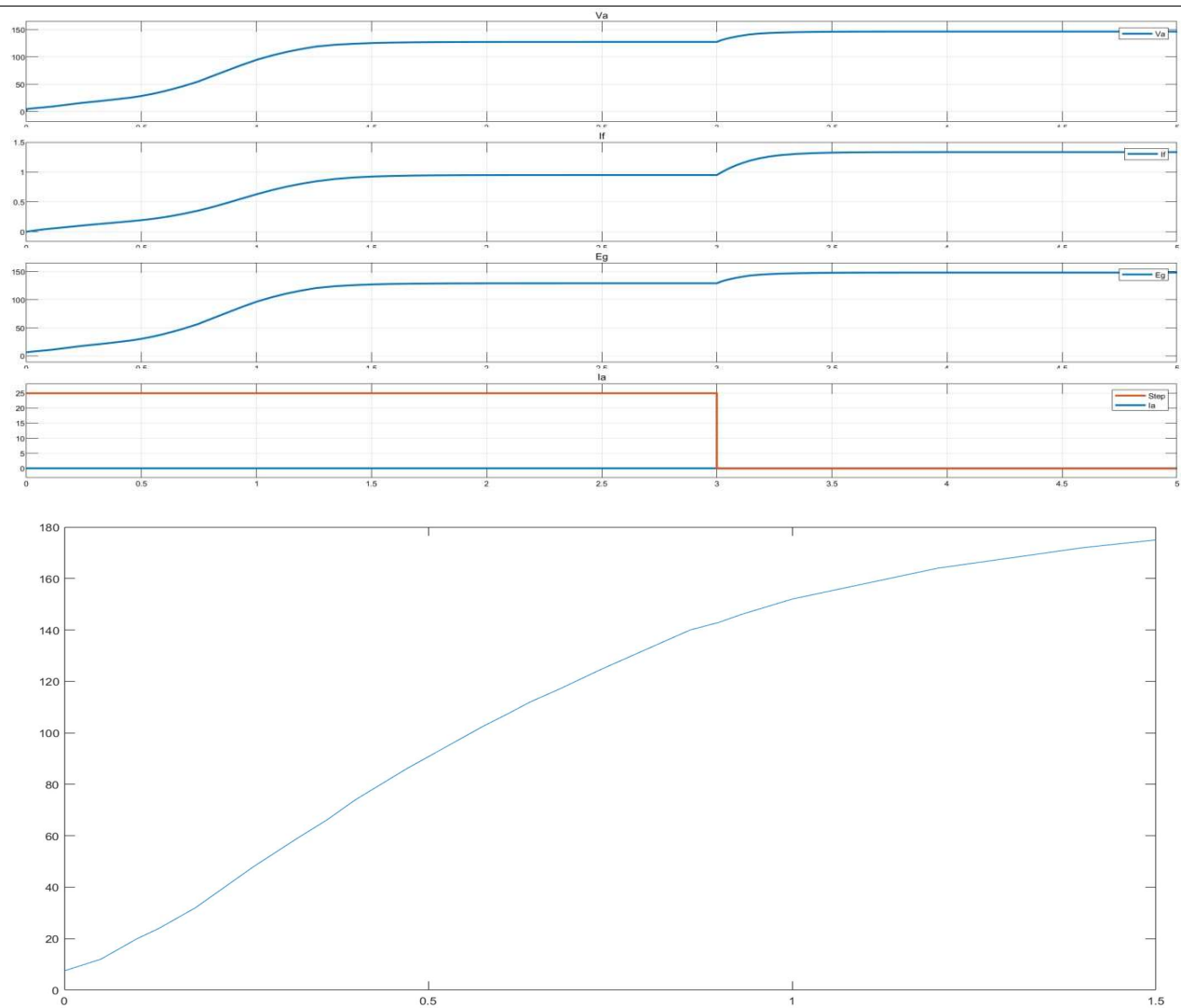

Simulation rendered waveforms

Comparison (Observations):

Hence, we were able to obtain the plots for dc shunt generator under magnetic saturation conditions.

Conclusion:

Hence, we were able to obtain the plots for dc shunt generator under magnetic saturation conditions.

Inference:

We were able to see the effects of armature reaction in a dc shunt generator

References: -NIL-